

C2 REVIEW ASSIGNMENT

CIRCUIT SIMULATIONS
WITH SPICE

TEJAS MESHARAM
MEC2021015

MTECH
1ST SEM ECE



Question 1

Find out the Voltage gain of the amplifier of the circuit shown in Fig.1. Choose the component and transistor parameters in the SPICE program. Choose the input DC bias. Provide the SPICE code and results (AC and Transient both).


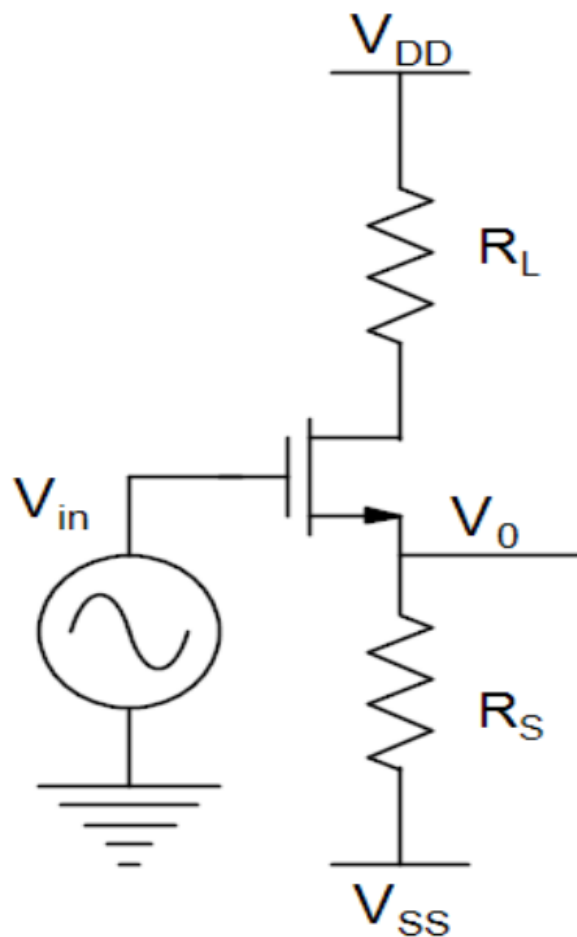


Fig.1: Schematic of Amplifier

Mentioning nodes for Fig.1

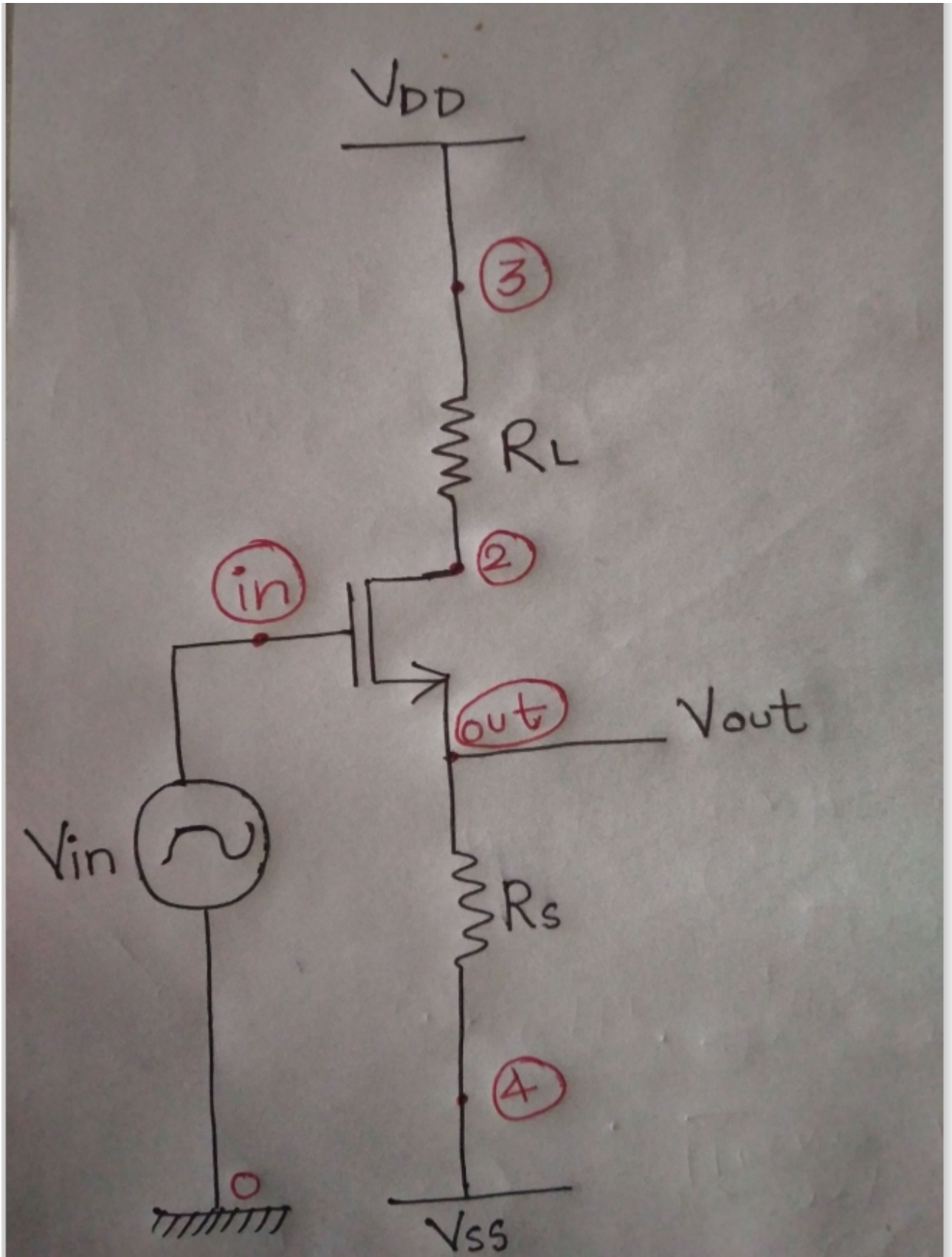

Solution 1

> WRITING THE NETLIST

```
***** Question 1 *****
```

```
Vin in 0 ac 1.0 sin(0.75 0.75 0.1khz 0 0)
```

```
Vdd 3 0 1.6
```

```
Vss 0 4 0.5
```

```
RL 2 3 12k
```

```
Rs out 4 5k
```

```
M1 2 in out 0 ntype l=180nm w=480nm
```

```
.plot ac Vdb(out,in)
```

```
.plot V(out) V(in)
```

```
.MODEL ntype NMOS ( LEVEL = 49
```

```
+VERSION = 3.1 TNOM = 27
```

```
+XJ = 1E-7 NCH = 2.3549E17
```

```
+K1 = 0.5826058 K2 = 6.016593E-
```

```
+K3B = 1.4046112 W0 = 1E-7
```

```
+DVT0W = 0 DVT1W = 0
```

```
+DVT0 = 1.3156832 DVT1 = 0.397759
```

```
+U0 = 280.5758609 UA = -1.208176E
```

```
+UC = 5.340577E-11 VSAT = 9.601364E4
```

```
+AGS = 0.4008594 B0 = -3.73715E-
```

```
+KETA = -1.136459E-3 A1 = 2.580625E-
```

> TRANSIENT ANALYSIS

Transient Analysis Parameters

Stepsize : 0.01

Final Time: 30m

Optional:

Display Start Time:


Maximum Stepsize:

☐ Use Initial Conditions (UIC)

Save

Run

Cancel

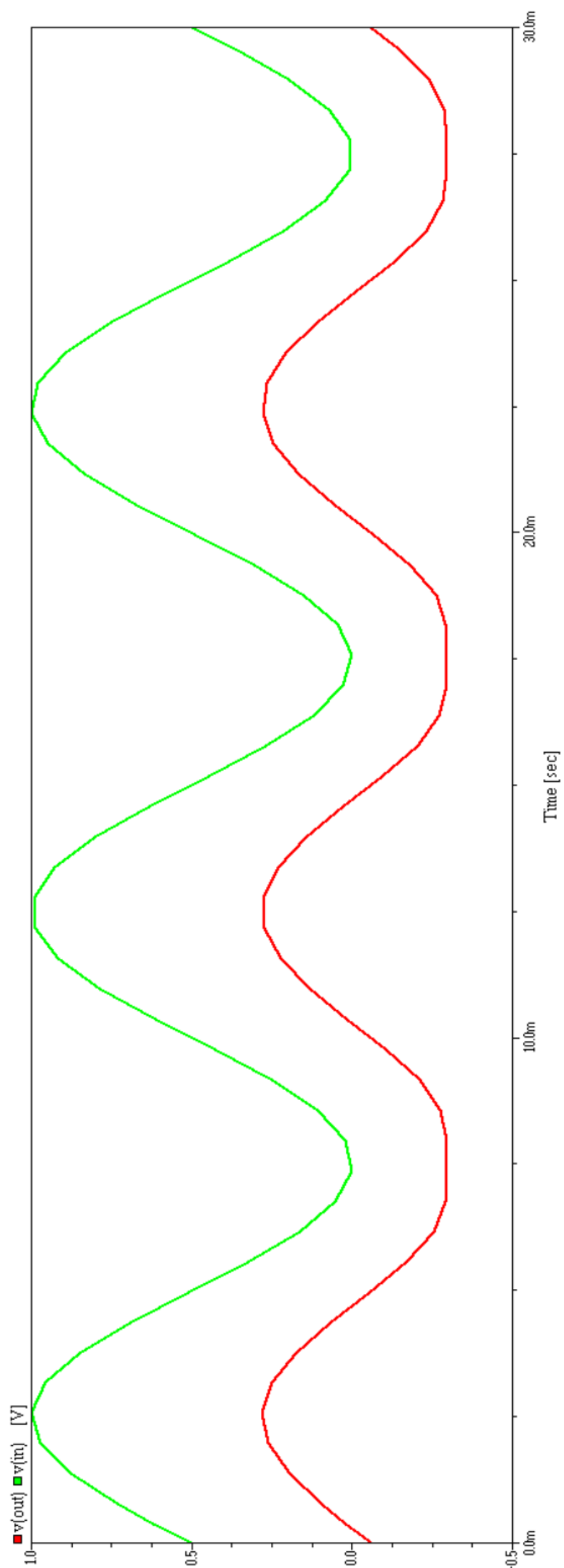

> AC output voltage gain analysis

AC Analysis Parameters

Sweep:

☐ LIN ☐ OCT ☒ DEC

Points/decade:

20

Start Frequency:

1k


End Frequency:

10G

Save

Run

Cancel

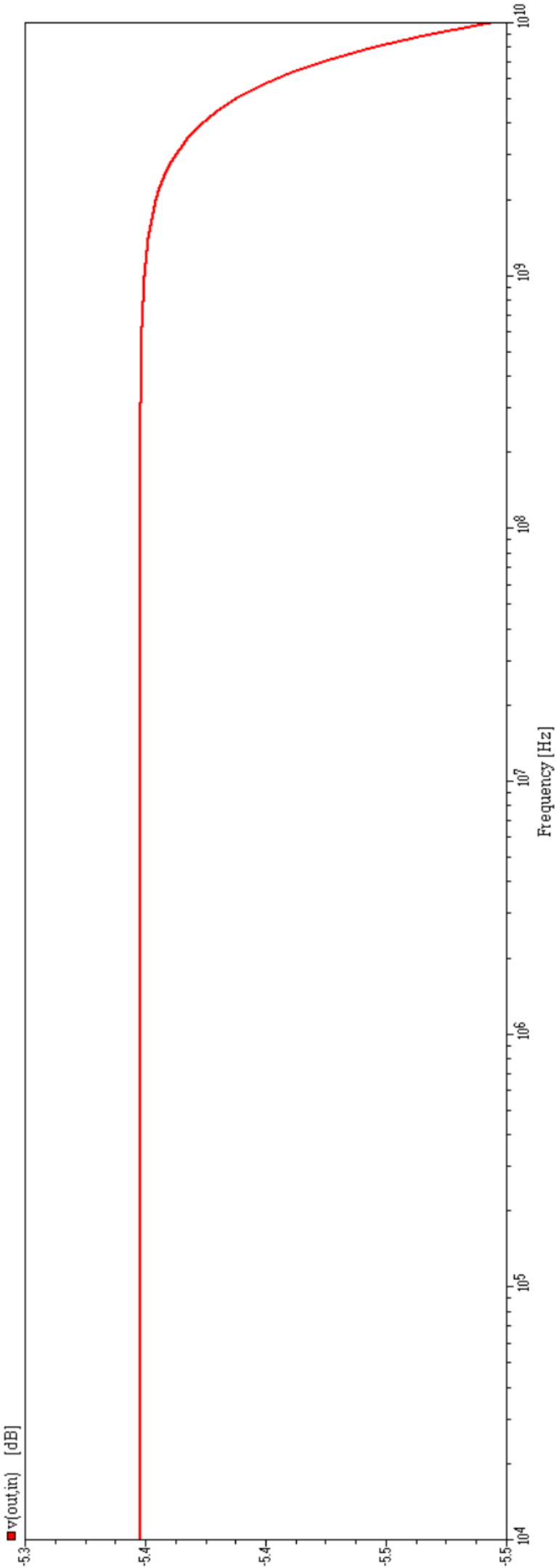

Question 2

Find out the Voltage gain of the amplifier of the circuit shown in Fig.2. Choose the component and transistor parameters in the SPICE program. Provide the SPICE code and results (AC and Transient both).


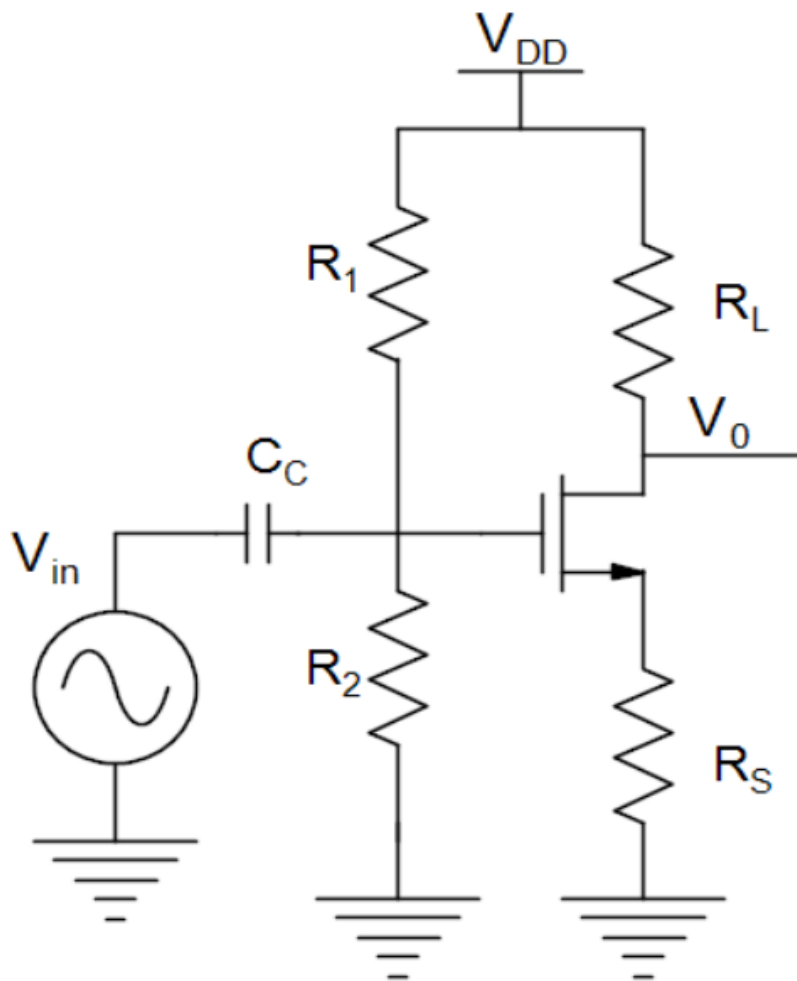


Fig.2: Schematic of Amplifier

Mentioning nodes for Fig.2

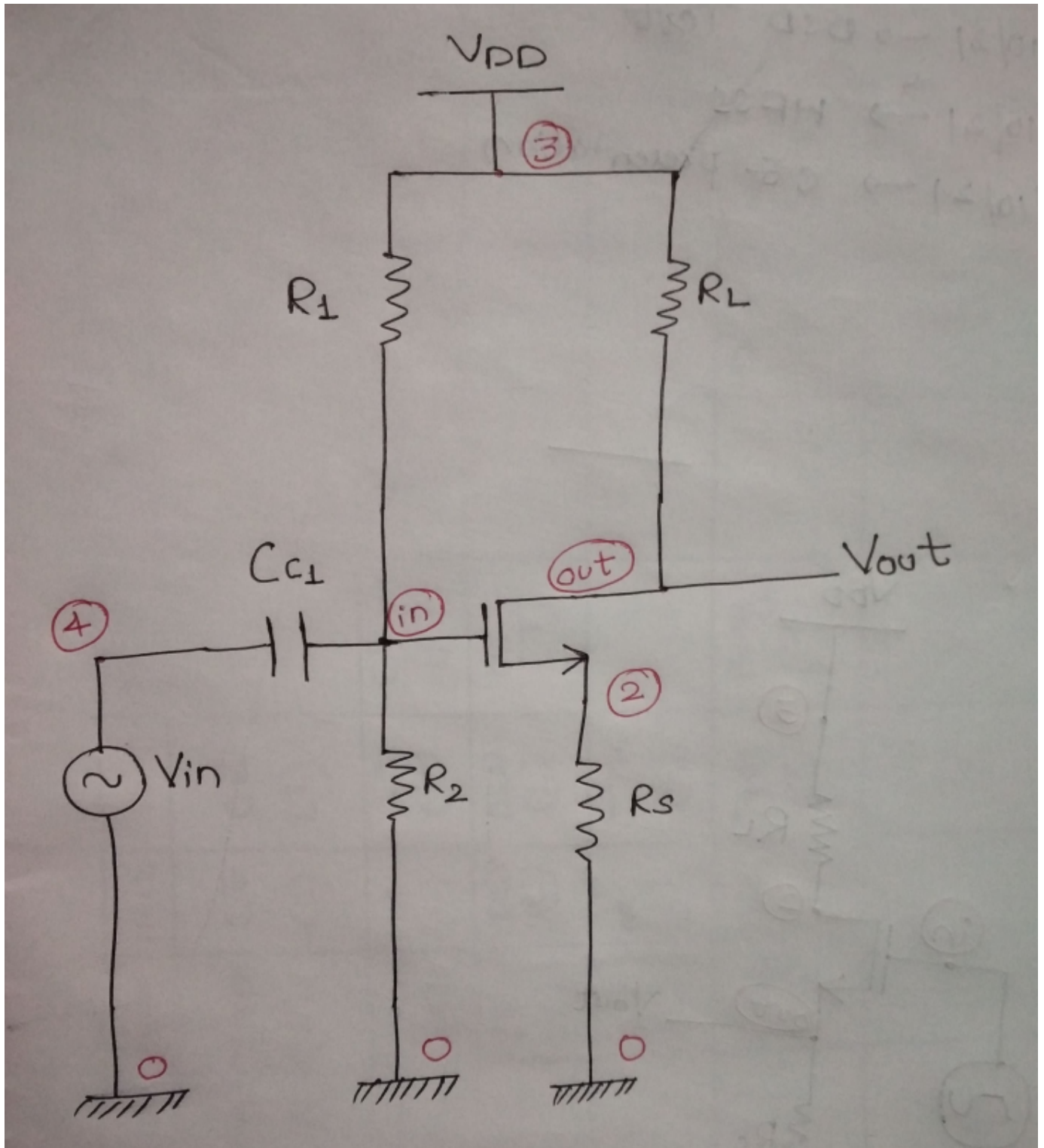

Solution 2

> WRITING THE NETLIST

```
***** Question 2 *****
```

```
Vdd 3 0 dc 1.6
```

```
Vin 4 0 dc 0.0 ac 1.0 sin(0.75 0.75 0.1khz 0 0)
```

```
R1 in 3 110k
```

```
R2 in 0 140k
```

```
RL out 3 4k
```

```
Rs 2 0 3.5k
```

```
M1 out in 2 0 ntype l=180nm w=480nm
```

```
Cc1 in 4 0.5
```

```
Cc2 out 0 5p
```

```
.plot ac vdb(out,in)
```

```
.plot v(out) v(in)
```

```
.MODEL ntype NMOS ( LEVEL = 49
```

```
+VERSION = 3.1 TNOM = 27
```

```
+XJ = 1E-7 NCH = 2.3549E17
```

```
+K1 = 0.5826058 K2 = 6.016593E-3
```

```
+K3B = 1.4046112 W0 = 1E-7
```

```
+DVT0W = 0 DVT1W = 0
```

```
+DVT0 = 1.3156832 DVT1 = 0.397759
```

```
+U0 = 280.5758609 UA = -1.208176E-9
```

```
+UC = 5.340577E-11 VSAT = 9.601364E4
```

```
+AGS = 0.4008594 B0 = -3.73715E-9
```

```
+KETA = -1.136459E-3 A1 = 2.580625E-4
```

```
+RDSW = 105.472458 PRWG = 0.5
```

> TRANSIENT ANALYSIS

Transient Analysis Parameters

Stepsize : 0.01

Final Time: 40m

Optional:

Display Start Time:


Maximum Stepsize:

☐ Use Initial Conditions (UIC)

Save

Run

Cancel

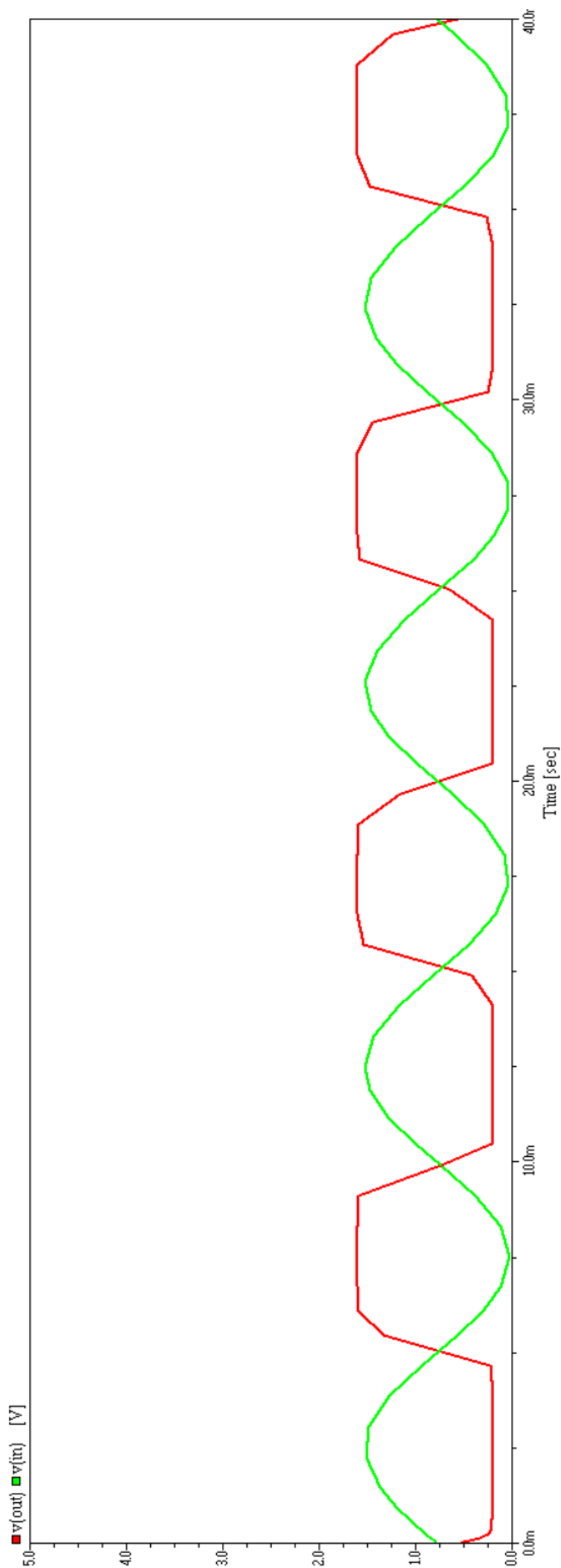

> AC output voltage gain analysis

AC Analysis Parameters

Sweep:

☐ LIN ☐ OCT ☒ DEC

Points/decade:

20

Start Frequency:

1k


End Frequency:

10G

Save

Run

Cancel

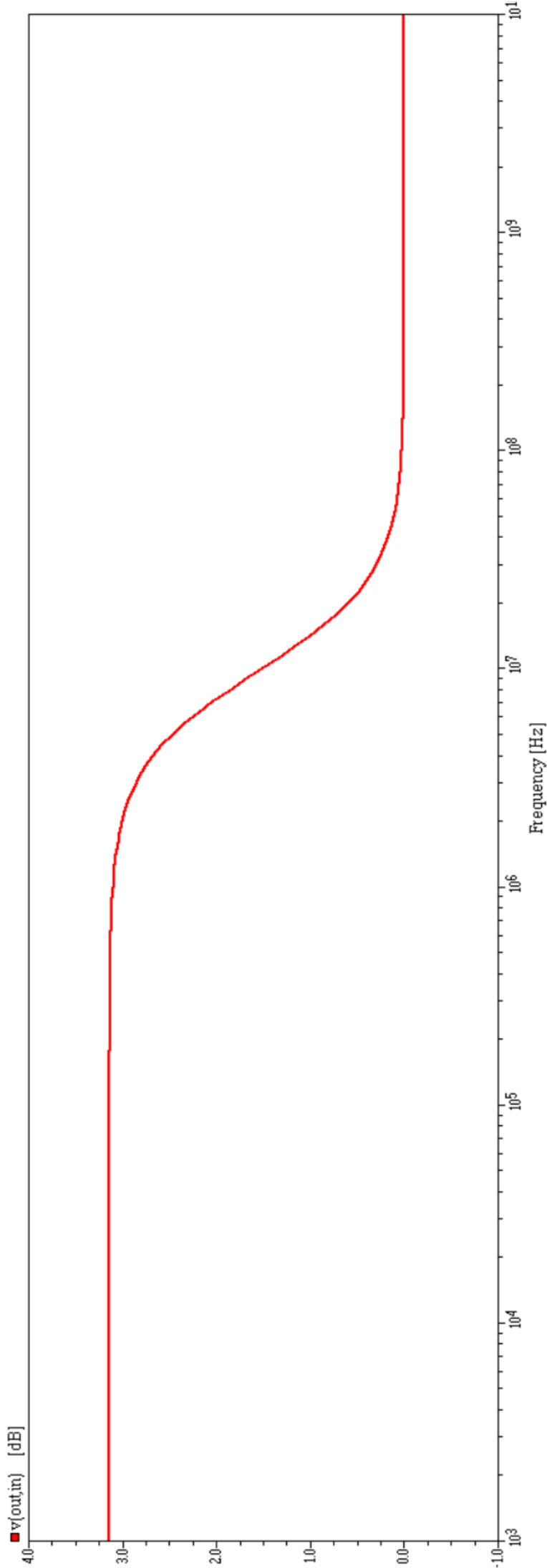

Question 3

Find out the Voltage gain of the amplifier of the circuit shown in Fig.3 by removing the coupling capacitor, C_C and incorporating negative bias. Choose the component and transistor parameters in the SPICE program. Provide the SPICE code and results (AC and Transient both).


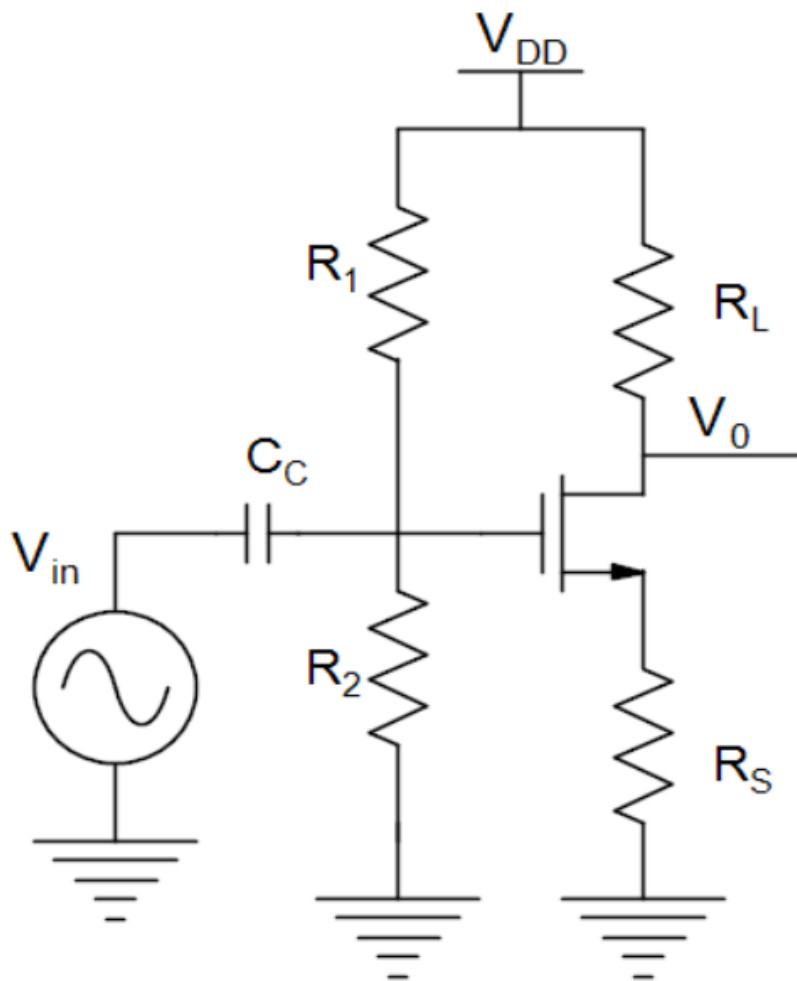


Fig.3: Schematic of Amplifier

Mentioning nodes for Fig.3

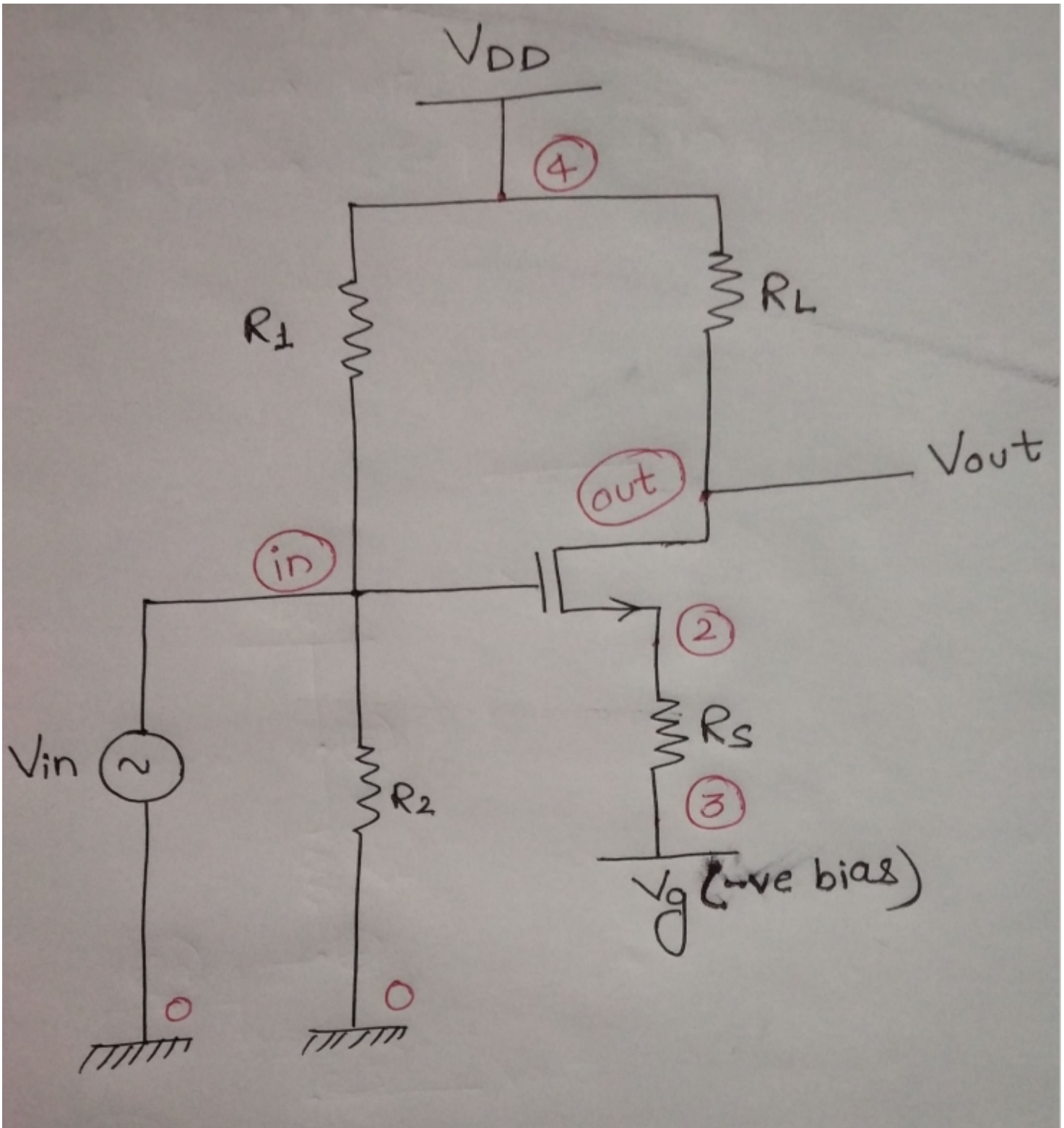

Solution 3

> WRITING THE NETLIST

```
***** Question 3 *****
```

```
Vdd 4 0 1.8
```

```
Vg 0 3 0.5
```

```
Vin in 0 dc 0.0 ac 1.0 sin(0.75 0.75 0.1khz 0 0)
```

```
R1 in 4 80k
```

```
RL out 4 2k
```

```
R0 in 0 30k
```

```
Rs 2 3 1.2k
```

```
M1 out in 2 0 ntype l=180nm w=480nm
```

```
Cc out 0 1f
```

```
.plot ac Vdb(out,in)
```

```
.plot v(out) v(in)
```

```
.Model ntype NMOS (LEVEL = 49
```

```
+VERSION = 3.1 TNOM = 27
```

```
+XJ = 1E-7 NCH = 2.3549E17
```

```
+K1 = 0.5826058 K2 = 6.016593E-3
```

```
+K3B = 1.4046112 W0 = 1E-7
```

```
+DVT0W = 0 DVT1W = 0
```

```
+DVT0 = 1.3156832 DVT1 = 0.39775|9
```

```
+U0 = 280.5758609 UA = -1.208176E-9
```

> TRANSIENT ANALYSIS

Transient Analysis Parameters

Stepsize : 0.01

Final Time: 40m

Optional:

Display Start Time:


Maximum Stepsize:

☐ Use Initial Conditions (UIC)

Save

Run

Cancel

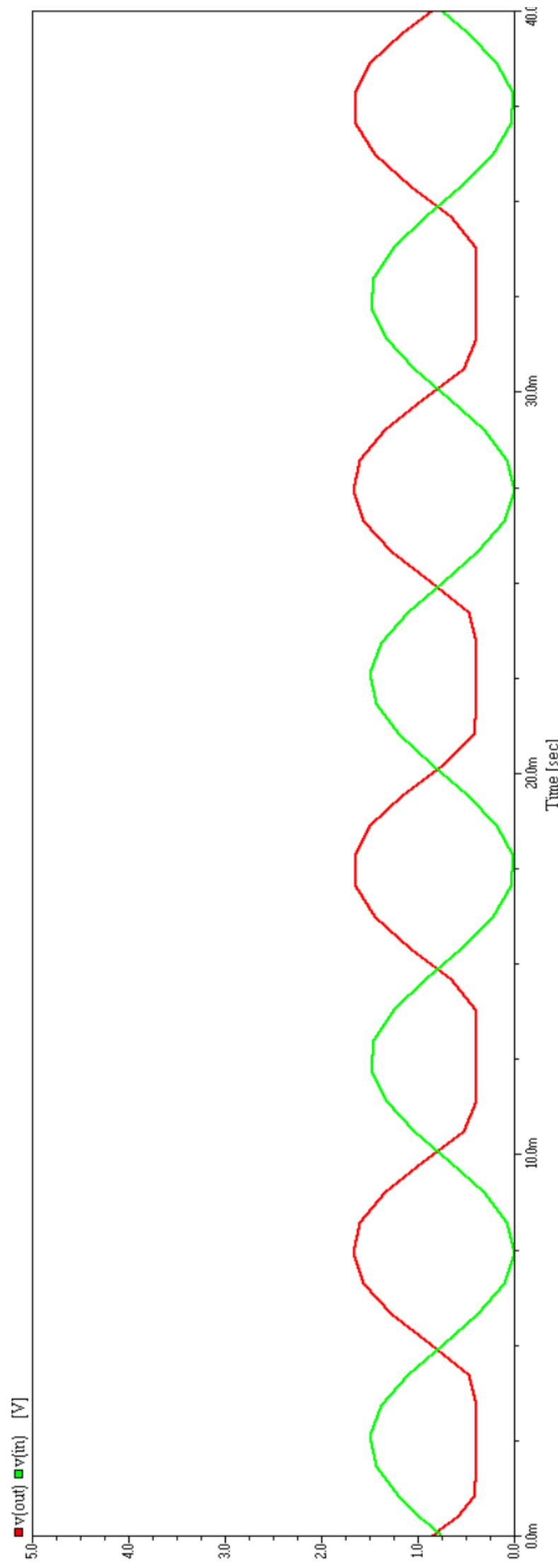

> AC output voltage gain analysis

AC Analysis Parameters

Sweep:

☐ LIN☐ OCT☒ DEC

Points/decade:

20

Start Frequency:

1k


End Frequency:

10G

Save

Run

Cancel

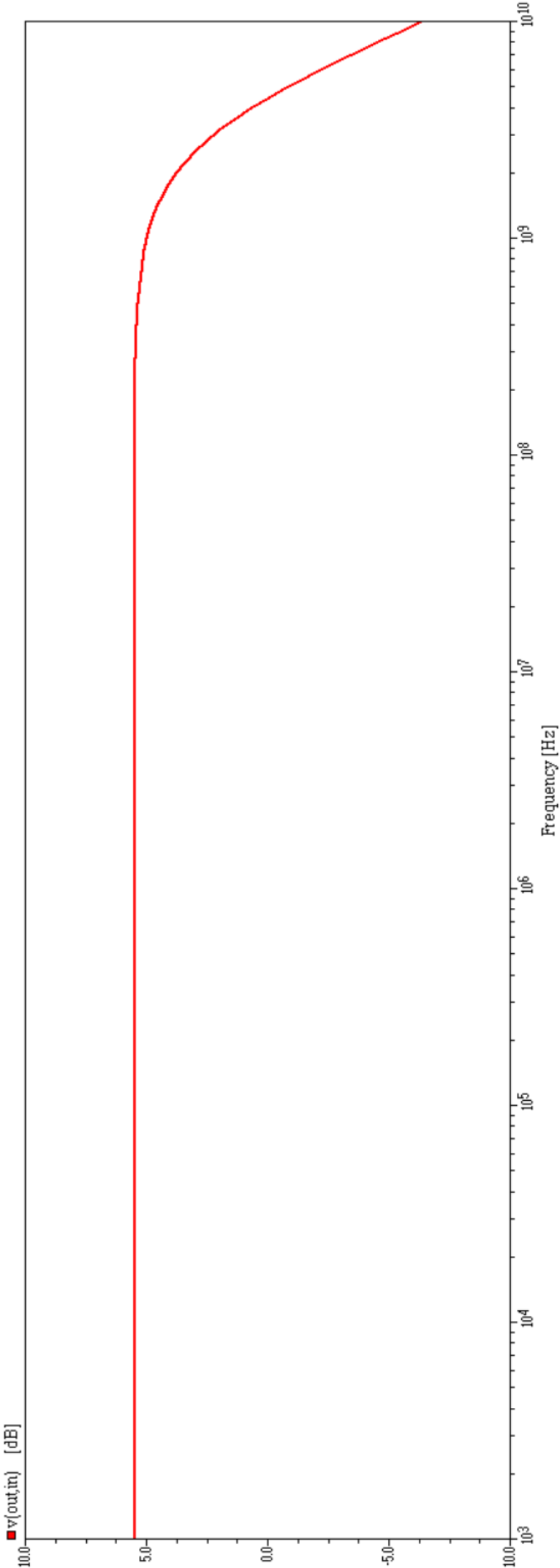

**You have reached end
of this document**

Thank you